
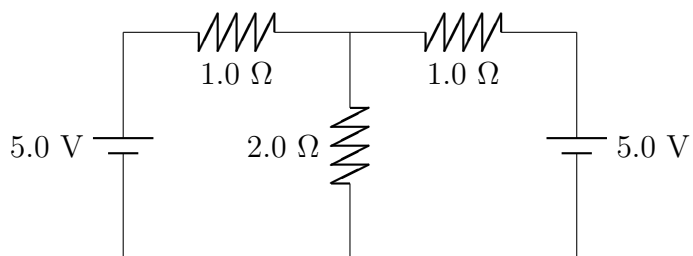


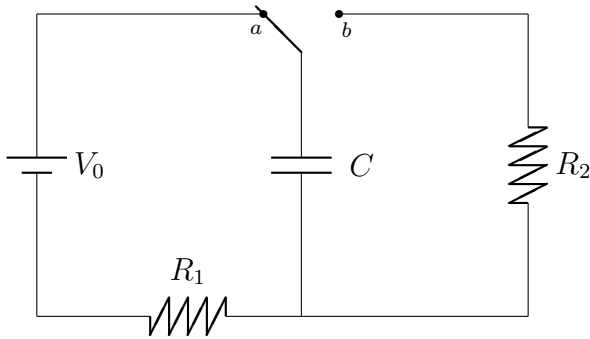1. (20 points) You have the following circuit. Calculate the voltage across, the current through, and the power dissipated by each resistor.




**2. (30 points)** Here is a simplified (oversimplified) model of a circuit for a camera flash. The resistance  $R_1$  is considerably larger than  $R_2$ . When the switch is at  $a$ , the capacitor  $C$  slowly recharges. When the switch is at  $b$ ,  $C$  rapidly discharges.



- (a) Say the switch remains at  $a$  for a long time in order to fully charge up the capacitor. This is a “long time” compared to what?
- (b) What is the power dissipated by  $R_2$  immediately after the switch is flipped to  $b$ ? Explain, using this, why a flash requires a small value for  $R_2$ .
- (c) Say  $C = 12 \mu\text{F}$ , and  $R_2 = 0.21 \Omega$ . How long will it take for the capacitor to discharge 90% of its starting charge?


**3. (50 points)** You have a capacitor (its capacitance is not important), a switch, wires, a 15.0 V DC battery, a  $5.0\ \Omega$  resistor, and a device that behaves like a  $10.0\ \Omega$  resistor.

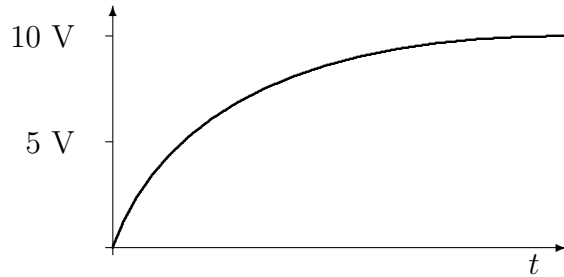- (a) You want the voltage across your device to behave like the following graph after you close the switch; starting at 0.0 V and gradually going up to 10.0 V:



Draw a circuit diagram for the circuit that will do this. Write the junction and loop equations and show that immediately after you close the switch and a long time after you close the switch, the voltage across your device will be 0.0 V and 10.0 V.

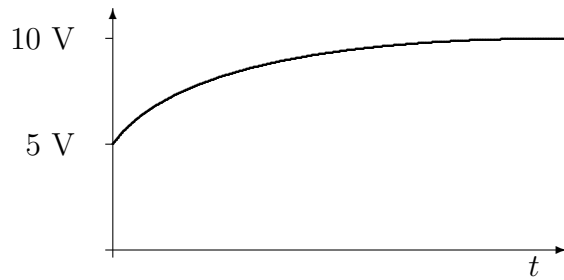- (b) Let's say that instead of the situation in (a), your device requires a voltage graph looking like the following, starting at 5.0 V and gradually going up to 10.0 V:



You can accomplish this by adding an extra resistor  $R$  to the circuit that you had for (a). Draw the circuit with the extra resistor  $R$ , and use loop and junction equations to calculate the value of  $R$  for which the voltage across the device will be 5.0 V immediately after closing the switch and 10.0 V a long time after.