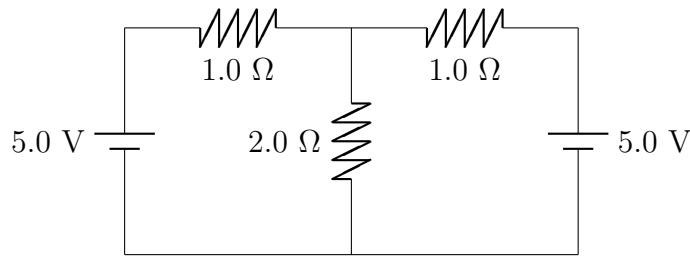


Solutions to Assignment 4; Phys 186


1. (20 points) You have the following circuit. Calculate the voltage across, the current through, and the power dissipated by each resistor.



Answer: Use loops and junctions. Or use this shortcut: the left and right halves of this circuit are identical. So clearly the currents through the $1\ \Omega$ resistors are identical: call them I_1 . Call the current through the $2\ \Omega$ resistance I_2 . The junction equation then becomes $I_2 = 2I_1$. Both loop equations are identical: $5\ \text{V} = (1\ \Omega)I_1 + (2\ \Omega)I_2$. Putting the equations together, we get $5\ \text{V} = (1\ \Omega)I_1 + (2\ \Omega)2I_1$, which means $I_1 = 1\ \text{A}$. Therefore $I_2 = 2\ \text{A}$.

The voltages: $V_1 = (1\ \Omega)I_1 = 1\ \text{V}$; $V_2 = (2\ \Omega)I_2 = 4\ \text{V}$. The powers: $P_1 = V_1I_1 = 1\ \text{W}$; $P_2 = V_2I_2 = 8\ \text{W}$.

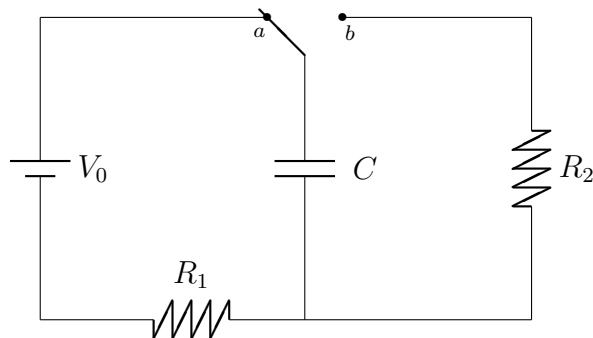2. (30 points) Here is a simplified (oversimplified) model of a circuit for a camera flash. The resistance R_1 is considerably larger than R_2 . When the switch is at a , the capacitor C slowly recharges. When the switch is at b , C rapidly discharges.



- (a) Say the switch remains at a for a long time in order to fully charge up the capacitor. This is a “long time” compared to what?

Answer: The time scale for charging up is R_1C —so the time must be long compared to R_1C .

- (b) What is the power dissipated by R_2 immediately after the switch is flipped to b ? Explain, using this, why a flash requires a small value for R_2 .

Answer: Since the capacitor was fully charged, the voltage across it immediately after the switch is flipped will be V_0 . (It would not have had any time to discharge yet.) Therefore, using a loop equation, the voltage across the resistor will also be V_0 and the current going through will be V_0/R_2 . The power is then

$$P = \frac{V_0^2}{R_2}$$

A flash requires a large burst of energy delivered in a short amount of time. Therefore P should be large—which is why R_2 should be small.

- (c) Say $C = 12 \mu\text{F}$, and $R_2 = 0.21 \Omega$. How long will it take for the capacitor to discharge 90% of its starting charge?

Answer: The capacitor needs to go down to $1 - 0.9 = 0.1$ of its original charge. Using the exponential discharge relationship,


$$Q = Q_0 e^{-t/R_2C} \quad \Rightarrow \quad \frac{Q}{Q_0} = 0.1 = e^{-t/R_2C}$$

Therefore

$$t = -R_2C \ln 0.1 = 5.8 \times 10^{-6} \text{ s}$$


3. (50 points) You have a capacitor (its capacitance is not important), a switch, wires, a 15.0 V DC battery, a 5.0 Ω resistor, and a device that behaves like a 10.0 Ω resistor.

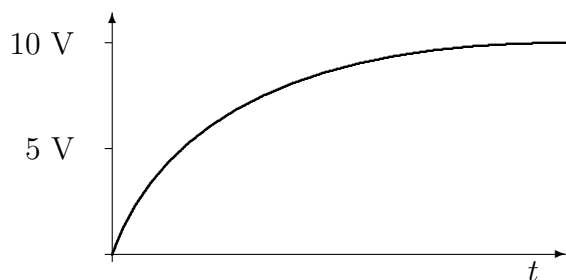- (a) You want the voltage across your device to behave like the following graph after you close the switch; starting at 0.0 V and gradually going up to 10.0 V:



Draw a circuit diagram for the circuit that will do this. Write the junction and loop equations and show that immediately after you close the switch and a long time after you close the switch, the voltage across your device will be 0.0 V and 10.0 V.

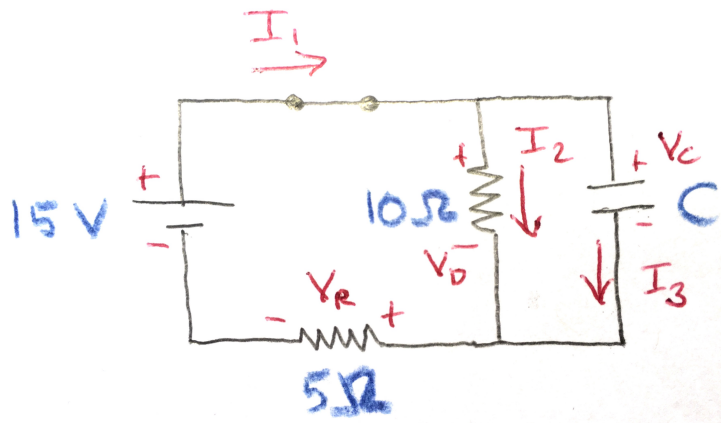Answer: Notice that the voltage graph looks exactly like that for a capacitor charging up. So you should connect your device in parallel with the capacitor, forcing them to have the same voltage. Circuit:




Junction: $I_1 = I_2 + I_3$. Loops: $15\text{ V} = V_D + V_R$ and $V_D = V_C$.

At $t = 0$, the capacitor still has no charge, so $V_C = 0$. Therefore $V_D = 0$ as well, which is what we want.


At large times, the capacitor will have fully charged up, so no current will go through it. Therefore $I_3 = 0$. Therefore $I_1 = I_2$ and $15\text{ V} = (10\ \Omega)I_1 + (5\ \Omega)I_1$, which means $I_1 = 1\text{ A}$ and $V_D = (10\ \Omega)I_1 = 10\text{ V}$.

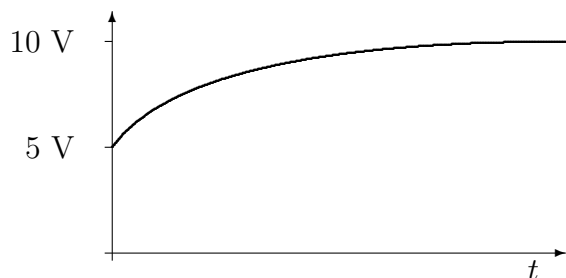- (b) Let's say that instead of the situation in (a), your device requires a voltage graph looking like the following, starting at 5.0 V and gradually going up to 10.0 V:



You can accomplish this by adding an extra resistor R to the circuit that you had for (a). Draw the circuit with the extra resistor R , and use loop and junction equations to calculate the value of R for which the voltage across the device will be 5.0 V immediately after closing the switch and 10.0 V a long time after.

Answer: Circuit:

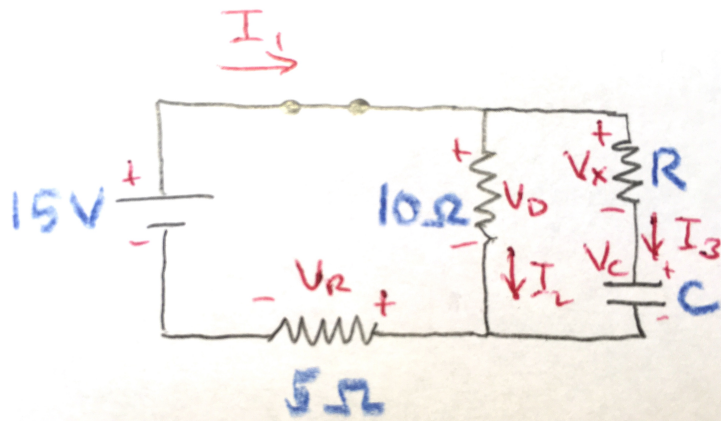

Junction: $I_1 = I_2 + I_3$. Loops: $15\text{ V} = V_D + V_R$ and $V_D = V_C + V_x$.

At $t = 0$, $V_C = 0$ again, plus we know that $V_D = 5\text{ V}$. Therefore $V_x = 5\text{ V}$ and $V_R = 10\text{ V}$. In that case, $I_1 = V_R/(5\ \Omega) = 2\text{ A}$, $I_2 = V_D/(10\ \Omega) = 0.5\text{ A}$. Using the junction equation, $I_3 = 2 - 0.5 = 1.5\text{ A}$. So $R = V_x/I_3 = 5/1.5 = 3.33\ \Omega$.

At large times, no current goes through the capacitor, which is exactly the same situation as in part (a), so as before, $V_D = 10\text{ V}$.