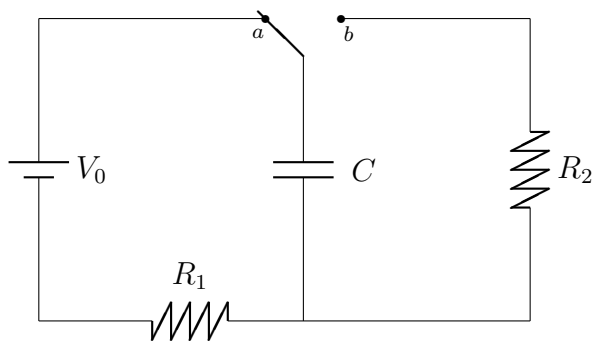



1. (20 points) Here is a simplified (oversimplified) model of a circuit for a camera flash. The resistance R_1 is considerably larger than R_2 . When the switch is at a , the capacitor C slowly recharges. When the switch is at b , C rapidly discharges.



- (a) Say the switch remains at a for a long time in order to fully charge up the capacitor. This is a “long time” compared to what?
- (b) What is the power dissipated by R_2 immediately after the switch is flipped to b ? Explain, using this, why a flash requires a small value for R_2 .
- (c) Say $C = 12 \mu\text{F}$, and $R_2 = 0.21 \Omega$. How long will it take for the capacitor to discharge 90% of its starting charge?


2. (30 points) You have a capacitor (its capacitance is not important), a switch, wires, a 15.0 V DC battery, a $5.0\ \Omega$ resistor, and a device that behaves like a $10.0\ \Omega$ resistor.

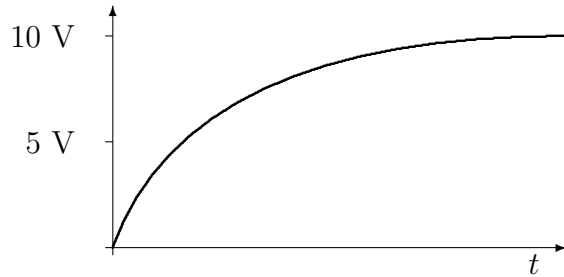- (a) You want the voltage across your device to behave like the following graph after you close the switch; starting at 0.0 V and gradually going up to 10.0 V:



Draw a circuit diagram for the circuit that will do this. Write the junction and loop equations and show that immediately after you close the switch and a long time after you close the switch, the voltage across your device will be 0.0 V and 10.0 V.

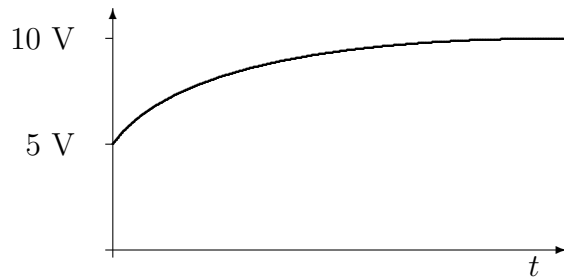- (b) Let's say that instead of the situation in (a), your device requires a voltage graph looking like the following, starting at 5.0 V and gradually going up to 10.0 V:




You can accomplish this by adding an extra resistor R to the circuit that you had for (a). Draw the circuit with the extra resistor R , and use loop and junction equations to calculate the value of R for which the voltage across the device will be 5.0 V immediately after closing the switch and 10.0 V a long time after.

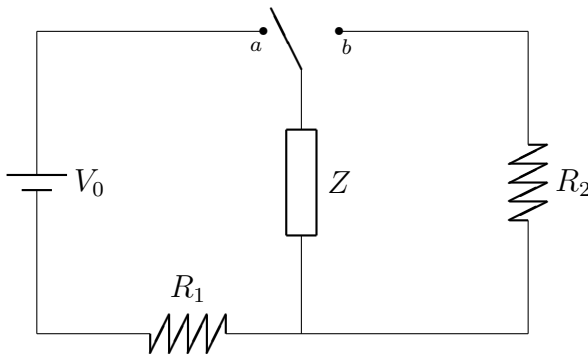3. (50 points) A capacitor stores energy in the electric field between its plates. It takes time for the field to change, so the voltage across a capacitor can't change instantaneously. But the current through a capacitor can change instantaneously, for example when you open or close a switch. All this means that if you have a capacitor with zero electric field, its voltage at that instant has to be zero, but its current can be anything. But when the electric field is at its maximum, the voltage across the capacitor will have the appropriate value, but the current now will have to be zero.


I now give you a device I will call a zingschritt. A zingschritt stores energy in the magnetic field in its coils. It takes time for the field to change, so the current through a zingschritt can't change instantaneously. But the voltage across a zingschritt can change instantaneously, for example when you open or close a switch. All this means that if you have a zingschritt with zero magnetic field, its current at that instant has to be zero, but its voltage can be anything. But when the magnetic field is at its maximum, the current through the zingschritt will have the appropriate value, but the voltage now will have to be zero.

You then have the following circuit that builds up or brings down the magnetic field in a zingschritt, depending on whether the switch is at position *a* or *b*. The rectangle represents your zingschritt.




(Questions start on the next page.)

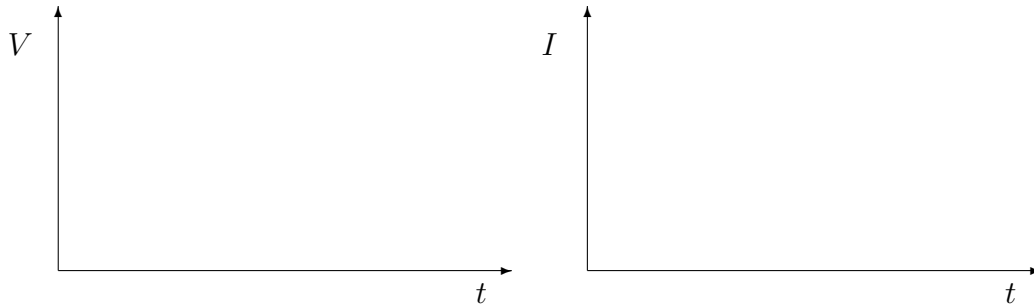
- (a) You start with no magnetic field in the zingschritt, with the switch neither connected to a nor b . Then you connect it to a . Immediately after the switch is set to a , what is the current through the zingschritt, and the voltage across the zingschritt? You then wait a long time, so that the magnetic field reaches its maximum value. What, then, is the current through the zingschritt, and the voltage across the zingschritt? Make rough sketches of how the voltage and current depend on time, with $t = 0$ as the time you set the switch to a . Explain your reasoning, or provide calculations.



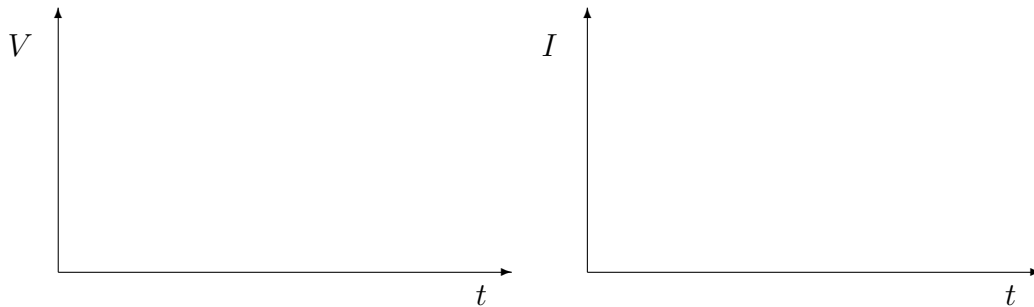- (b) After having built up the magnetic field in the zingschritt with the switch at a for a long time, you then flip the switch to b . Immediately after the switch is set to b , what is the current through the zingschritt, and the voltage across the zingschritt? You then wait a long time. What, then, is the current through the zingschritt, and the voltage across the zingschritt? Make rough sketches of how the voltage and current depend on time, with $t = 0$ as the time you set the switch to b . Explain your reasoning, or provide calculations.




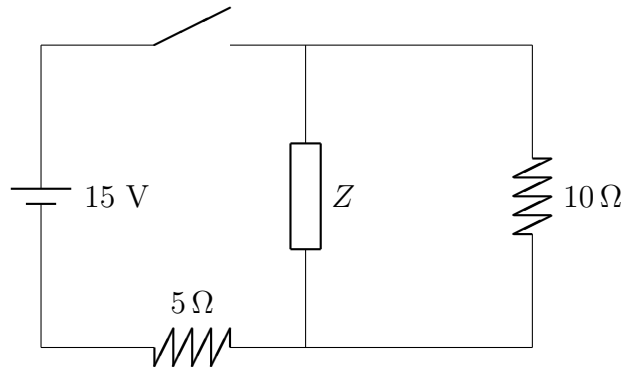- (c) You now have the following circuit, which includes a zingschritt. The switch has been open for a long time. You then close the switch at time $t = 0$. Calculate the voltage across the $10\ \Omega$ resistance at time $t = 0$, when the switch has just closed, and then the voltage after a long time has passed and the magnetic field in the zingschritt has reached its maximum value. Then sketch a graph of how the voltage across the $10\ \Omega$ resistance depends on time.



Extra Problems (not graded)

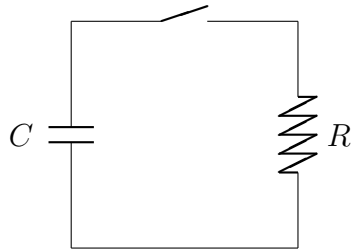4. (0 points) In the classroom, we discussed the following circuit for discharging a capacitor. The capacitor is fully charged at first, with voltage V_0 across it, when the switch is open; when the switch is closed at time $t = 0$, the charge starts to decline. We also discussed that since the current in the circuit after the switch is closed is due to the charges on the capacitor plates moving away, that the larger the current, the faster the capacitor will be discharged. Since a larger resistance R means a smaller current, the capacitor will take longer to discharge, with the current through the capacitor $I_C(t) = I_C(0) e^{-t/RC}$ and $I_C(0) = V_0/R$.




Now say you have two identical resistances, both R , which you hook up (1) in series, and (2) in parallel, and you replace your original R with these two two-resistor configurations.

- (a) Draw a diagram for each circuit, (1) and (2). Write down junction and loop equations for each circuit.

(b) Find expressions for $I_{C1}(0)$ and $I_{C2}(0)$, the currents through the capacitor at time $t = 0$ for each circuit, in terms of variables such as V_0 , R , and C . Which circuit, therefore, will discharge faster?

(c) Compare your result in (b) to the single- R circuit. All that has changed is the effective resistance values that appear in $I_C(0)$; after all, C is the same. So, by analogy, write down expressions for $I_{C1}(t)$ and $I_{C2}(t)$, for all times t . (Ask me for help if you need it!) Qualitatively sketch a graph of these two currents versus time, representing both currents on the same graph.

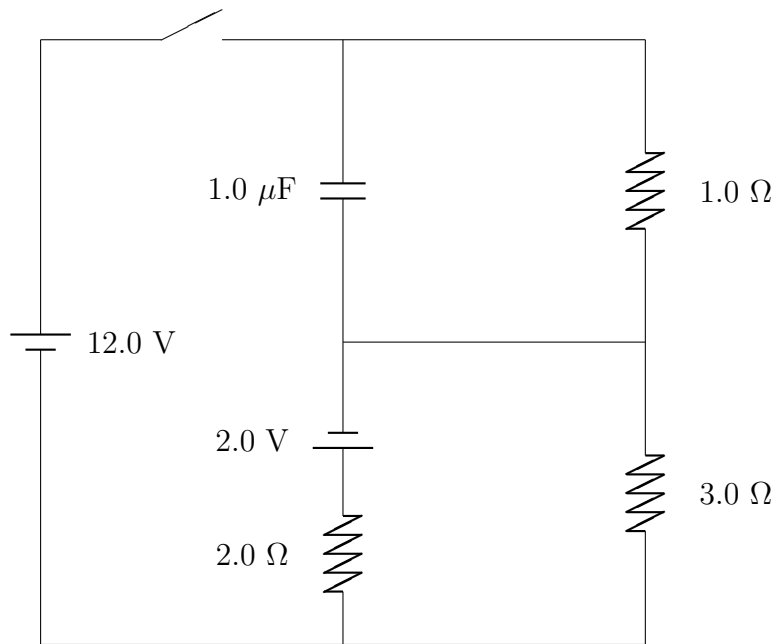5. (0 points) Just before the switch is closed, the capacitor in the following circuit is completely discharged. You then close the switch.



- (a) Find the currents through all the resistors *immediately after* the switch is closed, before the capacitor has any time to charge up at all.

- (b) Find the currents through all the resistors *a very long time after* the switch is closed, after the capacitor has completely charged up.

- (c) Sketch qualitative I vs t graphs for each of the currents. The switch closes at $t = 0$. (I_1 is the current through the $1\ \Omega$ resistor, I_2 is the current through the $2\ \Omega$ resistor, and I_3 is the current through the $3\ \Omega$ resistor.)

