

1. **(60 points)** You have a single-loop circuit with an AC voltage source $V_s = V_0 e^{i\omega t}$ together with a capacitor C , a resistor R , and an inductor L . The voltage across an inductor is $V_L = L dI/dt$. Set up the differential equation for Q , the charge on the capacitor. Solve for Q_p , the non-transient behavior, and also find I_p , the corresponding current.
2. **(40 points)** What is the resonance frequency for this circuit, where I_p is a maximum?