

PHYS 191 Activity 7: RC Circuits

Draw a single-loop circuit including a switch, voltage source V_s , resistance R , and capacitor C . At time $t = 0$, the switch will be closed.

1. Write down the loop equation relating the voltages across the source, resistance, and battery after the switch is closed. Then write the loop equation in the form of a differential equation for Q , the charge on the capacitor. Remember that $Q = CV_C$ and $V_R = RI$. What is the relationship between I and Q ?

Answer: The loop equation is $V_s = V_C + V_R$. Since the current in the circuit is entirely due to the charging and discharging of the capacitor, $I = \frac{dQ}{dt}$. Putting these together,

$$V_s = \frac{1}{C}Q + R\frac{dQ}{dt}$$

2. Say $V_s = 0$: this will be a discharge circuit for the capacitor. Solve the differential equation for the circuit in this case by direct integration—rearrange the equation until you have $\int dt$ (something) = $\int dQ$ (something) and you can take the integrals. Then, use the initial condition that at $t = 0$, the initial charge on the capacitor was Q_0 .

Answer: Rearranging the equation,

$$-\frac{1}{C}Q = R\frac{dQ}{dt} \quad \Rightarrow \quad -\frac{1}{C}dt = R\frac{dQ}{Q} \quad \Rightarrow \quad -\frac{1}{C}\int_{t_i}^t dt = R\int_{Q_i}^Q \frac{dQ}{Q}$$

Doing the integrals,

$$\frac{1}{C}(t - t_i) = R(\ln Q - \ln Q_i) \quad \Rightarrow \quad \frac{Q}{Q_i} = \exp\left(-\frac{t - t_i}{RC}\right) \quad \Rightarrow \quad Q = Q_0 e^{-t/RC}$$

The charge exponentially decays.

3. Say $V_s = V_0$, a constant. The solution of a *linear* differential equation can be written as $Q = Q_p + Q_h$. Here, Q_h is the solution to the equation with $V_s = 0$, including the undetermined multiplying constant. We already have this. We just need Q_p , a “particular solution” with no undetermined constants. What would be Q_p for the circuit with a constant voltage source? Try to guess—in this case it’s easy, even trivial.

Answer: A constant will work: $Q_p = CV_0$.

4. Write down the full solution for the case $V_s = V_0$, with no undetermined constants, using the initial condition that at $t = 0$, $Q = 0$.

Answer: The full solution is

$$Q = Q_p + Q_h = CV_0 + Q_0 e^{-t/RC}$$

At $t = 0$, we have $0 = CV_0 + Q_0$, therefore $Q_0 = -CV_0$. The solution is

$$Q = CV_0 (1 - e^{-t/RC})$$

This describes a circuit gradually charging a capacitor up to its maximum charge of CV_0 .

5. We now have an AC voltage, with $V_s = V_0 e^{i\omega t}$. What would Q_p be in this case? Remember the early weeks of the semester.

Answer: Try an exponential solution $Q_p = A e^{i\omega t}$.

$$V_0 e^{i\omega t} = \frac{1}{C} A e^{i\omega t} + iR\omega A e^{i\omega t} \quad \Rightarrow \quad A = \frac{CV_0}{1 + iRC\omega}$$

Note that A is complex and ω -dependent, indicating a frequency-dependent amplitude and also a frequency-dependent phase difference between the voltage and the charge (and current).

6. Write down the full solution for the AC RC circuit, with the initial condition that at $t = 0$, the initial charge on the capacitor was 0.

Answer: Combining the particular and “homogeneous” (or transient) solutions,

$$Q = \frac{CV_0}{1 + iRC\omega} e^{i\omega t} + Q_0 e^{-t/RC}$$

At $t = 0$, $0 = A + Q_0$, therefore $Q_0 = -A$, and

$$Q = \frac{CV_0}{1 + iRC\omega} (e^{i\omega t} - e^{-t/RC})$$

The exponential decay part typically quickly goes away, hence it’s called “transient.”