

1. (60 points) You have a single-loop circuit with an AC voltage source $V_s = V_0 e^{i\omega t}$ together with a capacitor C , a resistor R , and an inductor L . The voltage across an inductor is $V_L = L dI/dt$. Set up the differential equation for Q , the charge on the capacitor. Solve for Q_p , the non-transient behavior, and also find I_p , the corresponding current.

Answer: With $I = dQ/dt$, $dI/dt = d^2Q/dt^2$. So

$$V_0 e^{i\omega t} = L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C}$$

Seek exponential solutions: $Q_p = A e^{i\omega t}$:

$$V_0 e^{i\omega t} = -LA\omega^2 e^{i\omega t} + iRA\omega e^{i\omega t} + \frac{A e^{i\omega t}}{C} \Rightarrow A = \frac{CV_0}{1 - LC\omega^2 + iRC\omega}$$

The current is

$$I_p = \frac{d}{dt}Q_p = \frac{i\omega CV_0}{1 - LC\omega^2 + iRC\omega} e^{i\omega t}$$

2. (40 points) What is the resonance frequency for this circuit, where I_p is a maximum?

Answer: Find the maximum by setting $\partial|I_p|/\partial\omega = 0$. Setting $\partial|I_p|^2/\partial\omega = 0$ will also work, and is slightly easier:

$$\frac{\partial|I_p|^2}{\partial\omega} = \frac{\partial}{\partial\omega} \left[\frac{\omega^2 C^2 V_0^2}{(1 - LC\omega^2)^2 + R^2 C^2 \omega^2} \right] = 0 \Rightarrow \omega = \frac{1}{\sqrt{LC}}$$

Note that the resonance frequency does not depend on R .